

# Two-Ports in Electrical Circuits

Gareth Williams, Ph.D.

Mathematics and Computer Science Department,  
Stetson University

Many electrical networks are designed to accept signals at certain points and to deliver a modified version of the signals. The usual arrangement is illustrated in Figure 1.

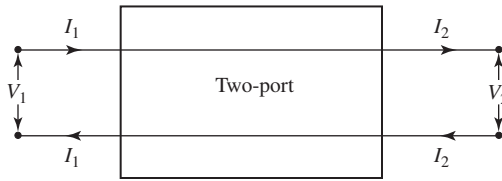


Figure 1 Electrical network

A current  $I_1$  at voltage  $V_1$  is delivered into a two-port, and it determines in some way the output current  $I_2$  at voltage  $V_2$ . In practice, the relationship between the input and output currents and voltages is usually linear—they are related by a matrix equation:

$$\begin{pmatrix} V_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}.$$

The coefficient matrix  $\begin{pmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{pmatrix}$  is called the **transmission matrix** of the port. This matrix defines the two-port.

Figure 2 is an example of a two-port. The interior consists of a resistance  $R$  connected as shown. Let us

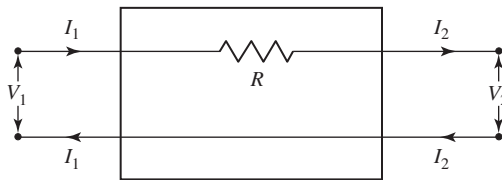


Figure 2 Two-port

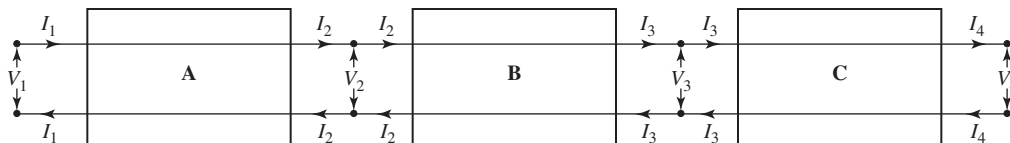


Figure 3 Two-ports in series

show that the currents and voltages do, indeed, behave in a linear manner and determine the transmission matrix. Our approach will be to construct two equations: one expressing  $V_2$  in terms of  $V_1$  and  $I_1$ , and the other expressing  $I_2$  in terms of  $V_1$  and  $I_1$ . We will then combine these two equations into a single matrix equation.

We use the following law:

**Ohm's law:** The voltage drop across a resistance is equal to the current times the resistance.

The voltage drop across the resistance is  $V_1 - V_2$ . The current through the resistance is  $I_1$ . Thus Ohm's law implies that  $V_1 - V_2 = I_1 R$ . The current  $I_1$  passes through the resistance  $R$  and exits as  $I_1$ . Thus  $I_2 = I_1$ . We write these two equations first in the standard form,

$$V_2 = V_1 - RI_1$$

$$I_2 = 0V_1 + I_1$$

and then as a single matrix equation,

$$\begin{pmatrix} V_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} 1 & -R \\ 0 & 1 \end{pmatrix} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}.$$

The transmission matrix is  $\begin{pmatrix} 1 & -R \\ 0 & 1 \end{pmatrix}$ . Thus, if  $R$  is 2 ohms and the input voltage and current are  $V_1 = 5$  volts and  $I_1 = 1$  amp, respectively, we get

$$\begin{pmatrix} V_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} 1 & -2 \\ 0 & 1 \end{pmatrix} \begin{pmatrix} 5 \\ 1 \end{pmatrix} = \begin{pmatrix} 3 \\ 1 \end{pmatrix}.$$

The output voltage and current are 3 volts and 1 amp, respectively.

In practice, a number of standard two-ports such as the one described above are placed in series to provide a desired voltage and current change. Consider the three two-ports of Figure 3, with transmission matrices **A**, **B**, and **C**.

Considering each port separately, we have

$$\begin{pmatrix} V_2 \\ I_2 \end{pmatrix} = \mathbf{A} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}, \quad \begin{pmatrix} V_3 \\ I_3 \end{pmatrix} = \mathbf{B} \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}, \quad \begin{pmatrix} V_4 \\ I_4 \end{pmatrix} = \mathbf{C} \begin{pmatrix} V_3 \\ I_3 \end{pmatrix}.$$

Substituting  $\begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$  from the first equation into the second gives

$$\begin{pmatrix} V_3 \\ I_3 \end{pmatrix} = \mathbf{BA} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}.$$

Substituting this last matrix  $\begin{pmatrix} V_3 \\ I_3 \end{pmatrix}$  into the third equation gives

$$\begin{pmatrix} V_4 \\ I_4 \end{pmatrix} = \mathbf{CBA} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}.$$

Thus the three ports are equivalent to a single two-port. The transmission matrix of this two-port is the product **CBA** of the individual ports. Note that the placement of each port in the sequence is important because matrices are not commutative under multiplication.

### Related Problems

In Problems 1–3, determine the transmission matrices of the two-ports in the given figure.

- $V_1 = V_2$  because terminals are connected directly. Current through resistance  $R$  is  $I_1 - I_2$ . Drop in voltage across  $R$  is  $V_1$ .

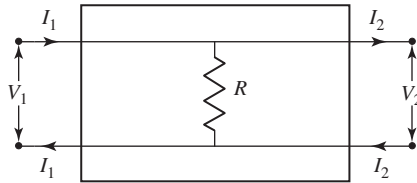


Figure 4 Two-port for Problem 1

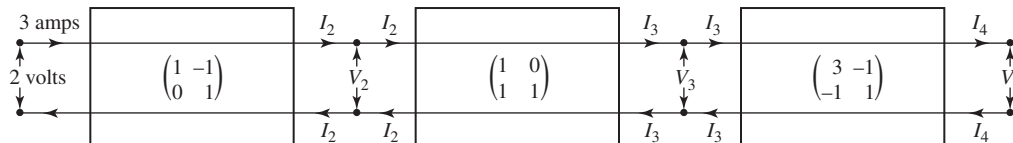


Figure 7 Two-ports in series for Problem 4

- Current through  $R_1$  is  $I_1 - I_2$ . Drop in voltage across  $R_1$  is  $V_1$ . Current through  $R_2$  is  $I_2$ . Drop in voltage across  $R_2$  is  $V_1 - V_2$ .

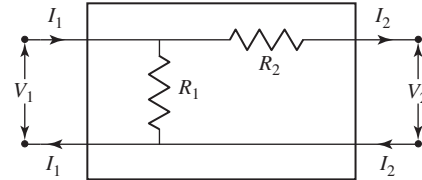


Figure 5 Two-port for Problem 2

- Current through  $R_1$  is  $I_1$ . Drop in voltage across  $R_1$  is  $V_1 - V_2$ . Current through  $R_2$  is  $I_1 - I_2$ . Drop in voltage across  $R_2$  is  $V_2$ .

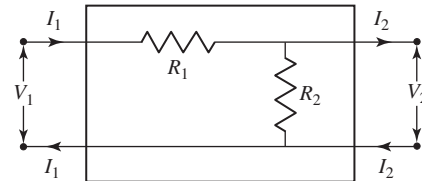


Figure 6 Two-port for Problem 3

- The two-port in Figure 7 consists of three two-ports placed in series. The transmission matrices are indicated.
  - What is the transmission matrix of the composite two-port?
  - If the input voltage is 3 volts and current is 2 amps, determine the output voltage and current.